Brown't kung adder is a logarithmic tree adder which uses the scheme of carry look ahead addition. But unlike carry look ahead adder, it does not look ahead all the way to the last bit in a single step because the complexity and delay will be inose. Instead it was used propagation and generation values in a tree like fashion where in each row we will have 2^n , 2^{n-1} , 2^{n-2} ... upto 2^0 blocks where $n = \log_2(no \cdot g)$ bis in adder). First, we will know, what carry look addernmeans.

suppose, we have A,B, cin bib to be added

If A=1,B=1 is respective of cin, cour will be 1.

So it is generation a= A.B. If B, A=1,0 or 0,1

the input carry should be propagated to cout so

if is propagation P= ABB. if A=0,B=0 cout=0 is represented of cin. So it is carry kill. k=AB but it

is not needed readly.

the next carry like citi = aitPic; -> 1st order

citi = aitPi(aintPincin) = (aitPiain)t(Pi.Pin)cin

citi can be generated by cin. so Piu here are 2nd order.

There terms will be cleared by the Bollowing diastam.

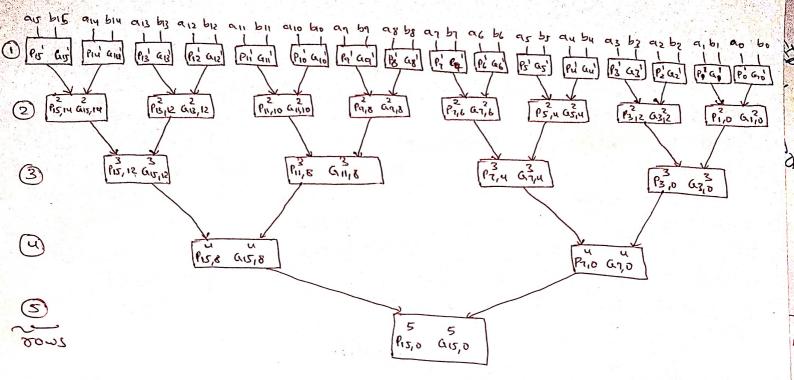


Fig1: Logarithmic propagation and generation computation

In the above figure, we can see for 16 bit brent kung adder propagation and generation signally are computed in logarithmic a tree fashion i.e; 2, 2, 2, 2 -3, 2 -

1st row —) 1st order propagation (p) and generation (a) values

2nd row —) 2nd order P, a, values

um row —) um order P, a values

sm row —) 5m order P, a values

sm row —) 5m order P, a values

Basically we know carry look ahead Generation my the

Citi= Pici+ ai = ai+Pici

carry so we can write citi of

so by using 2nd order pla volves we can compute citi from ci-1 directly without using ci. That meany we can skip internal carrier if we have the highest order P. a values. And here the beauty is all Pia values of every order is independent of input carries and can be computed even before the carry arrives. The carry is always in the critical path as it has to sipple through all the blocky in ripple carry adder, so that is why we are more concerned about cally rather than sum in Brent king adder it all comics are generated, we can compute sum by | sum = Ai (Bi (Ci) In this project, delay of Brent-kung-added is compared

with ripple carry adder critical delay.

once, all pla reims of volious order are known, we can compute the carry outputs which depend on co available at t=0.

C1 = $\frac{1}{16}$ + $\frac{1}{16}$ $\frac{$

so belically if we want to compute on we get logarithmic causing like (1,12,14,18,16 and from co by wing 1st, 2nd, 3od, um, 5m order plu respectively

perecated from cz, cu, cs, cu, cs, cs respectively by wing 1st order, 1st order, 1st order, 2nd order, 2nd order, 2nd order, 2nd order, 2nd order, 2nd order,

After this, we ger compute <1, <11, <13, <14

From <6, <10, <12, <12 by wing 1st order, fit order


first order, 2nd order respectively.

from 1st order. There are one after another of some one dependant on other.

By generating all counier, corresponding

Sums can be generated by sum; = p; (+) c; note: we can't generate an carrier at same time because some internal causes are dependent on omer. see the Rig 1. For understanding.

Waveforms for Brent kung adder

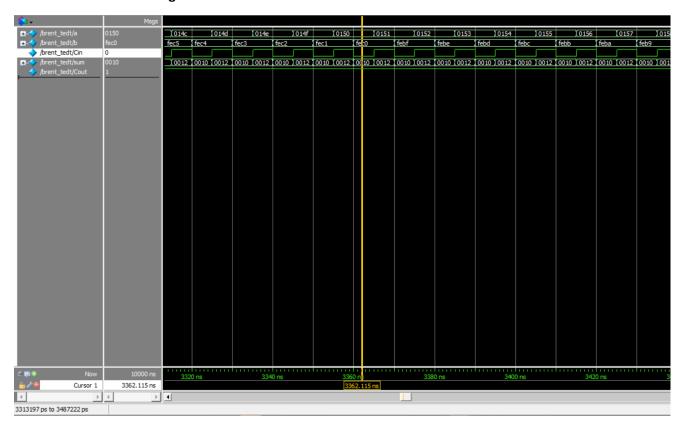

Maximum combinational Delay for Brent kung adder

```
Timing Detail:
All values displayed in nanoseconds (ns)
Timing constraint: Default path analysis
Total number of paths / destination ports: 633 / 17
                    18.582ns (Levels of Logic = 11)
Delay:
                     a<4> (PAD)
 Source:
                    Cout (PAD)
 Destination:
  Data Path: a<4> to Cout
                                          Net
                                 Gate
                     fanout Delay Delay Logical Name (Net Name)
    Cell:in->out
                  7 0.715 1.201 a_4_IBUF (a_4_IBUF)
                           1 0.479 0.740 Carry_8_or000054 (Carry_8_or000054)
     LUT2: T0->0
     LUT4:I2->0
                           1 0.479 0.976 Carry 8 or000063 (Carry 8 or000063)
                          3 0.479 0.794 Carry_8_or000076 (Carry_8_or000076)
     LUT4:I0->0
                           1 0.479 0.851 Carry 12 or000011 SW0 (N32)
1 0.479 0.740 Carry 12 or000031 SW1 (N42)
     LUT4:I3->0
     LUT4:I1->0
     LUT3:12->0
                          4 0.479 1.074 Carry_12_or000031 (Carry<12>)
                          1 0.479 0.851 Carry_16_or000011_SW0 (N30)
1 0.479 0.740 Carry_16_or000031_SW1 (N40)
1 0.479 0.681 Carry_16_or000031 (Cout_OBUF)
     LUT4:I0->0
     LUT4:I1->0
     LUT3:12->0
                                                Cout OBUF (Cout)
     OBUF:I->O
                                4.909
                              18.582ns (9.935ns logic, 8.647ns route)
    Total
                                         (53.5% logic, 46.5% route)
```

The delay for 16 bit ripple carry adder is also provided to compare how fast Brent kung adder is.

Maximum combinational Delay for ripple carry adder

```
All values displayed in nanoseconds (ns)
Timing constraint: Default path analysis
Total number of paths / destination ports: 321 / 17
 elay: 28.74lns (Levels of Logic = 18)
Source: b<0> (PAD)
Destination: cout (PAD)
Delay:
 Data Path: b<0> to cout
                                 Net
                         Gate
                fanout Delay Delay Logical Name (Net Name)
   Cell:in->out
                    2 0.715 1.040 b 0 IBUF (b 0 IBUF)
    IBUF: I->O
   2 0.479 0.915 ripple_gen[0].fl/cout1 (carry<1>)
   _____
                     28.74lns (13.288ns logic, 15.453ns route)
   Total
                               (46.2% logic, 53.8% route)
```

From the dealys, we can see Brent kung adder is fast compared to ripple carry adder.

The device specifications used for both synthesis of ripple carry adder and brent kung adder are given below

